

## Lab 9-10 – Nano processor Design Competition

### CS1050 Computer Organization and Digital Design

Dept. of Computer Science and Engineering, University of Moratuwa

210175C – G.G.T.A. Gamage

210429K - NINDUWARA K.G.M.

---

#### 1. Lab Task

Design a 4-bit processor capable of executing 4 instructions. The objective of this lab is to develop a 4-bit arithmetic unit that can perform addition and subtraction operations on signed integers. Additionally, we will design and develop the necessary components, such as instruction decoders, k-way b-bit multiplexers, and tri-state busses, to enable instruction execution.

#### 2.

MOVI R2, 3	10 010 000 0011
MOVI R7, 0	10 111 000 0000
MOVI R4, -1	10 100 000 1110
ADD R7, R2	00 111 010 0000
ADD R2, R4	00 010 100 0000
JZR R2, 8	11 010 0000 111
JZR R0, 4	11 000 0000 100
ADD R7, R0	00 111 000 0000

#### 3. VHDL Codes

##### Nano Processor

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date: 06/06/2023 02:47:24 PM
```

```

-- Design Name:
-- Module Name: NanoProcessor - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

ENTITY NanoProcessor IS
    PORT (
        Clk : IN STD_LOGIC;
        Res : IN STD_LOGIC;
        Zero : OUT STD_LOGIC;
        Overflow : OUT STD_LOGIC;
        S_7Seg : OUT STD_LOGIC_VECTOR(6 DOWNTO 0);
        OUT_REG : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
        Anode : out STD_LOGIC_VECTOR (3 downto 0)
    );
END NanoProcessor;

ARCHITECTURE Behavioral OF NanoProcessor IS
    COMPONENT InstructionDecoder PORT (
        Instruction : IN STD_LOGIC_VECTOR (11 DOWNTO 0);
        Jump_sel : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
        Imd_val : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
        Reg_en : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);
        Reg_selA : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);
    );

```

```

Load_sel : OUT STD_LOGIC;
Reg_selB : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);
--MUX_EN_A : OUT STD_LOGIC;
--MUX_EN_B : OUT STD_LOGIC;
REG_BANK_EN : OUT STD_LOGIC;
--Mux_2_to_1_EN : OUT STD_LOGIC;
Add_sub_sel : OUT STD_LOGIC;
Jump_address : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);
Jump : OUT STD_LOGIC);
END COMPONENT;

```

```

COMPONENT PC PORT (
    D_in : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
    Res : IN STD_LOGIC;
    Clk : IN STD_LOGIC;
    Q_out : OUT STD_LOGIC_VECTOR (2 DOWNTO 0));
END COMPONENT;

```

```

COMPONENT Add_Sub PORT (
    M : IN STD_LOGIC;
    A0 : IN STD_LOGIC;
    A1 : IN STD_LOGIC;
    A2 : IN STD_LOGIC;
    A3 : IN STD_LOGIC;
    B0 : IN STD_LOGIC;
    B1 : IN STD_LOGIC;
    B2 : IN STD_LOGIC;
    B3 : IN STD_LOGIC;
    S0 : OUT STD_LOGIC;
    S1 : OUT STD_LOGIC;
    S2 : OUT STD_LOGIC;
    S3 : OUT STD_LOGIC;
    Zero_flag : OUT STD_LOGIC;
    Sign_flag : OUT STD_LOGIC;
    Overflow_flag : OUT STD_LOGIC;
    Carry_flag : OUT STD_LOGIC
);
END COMPONENT;

```

```

COMPONENT adder_3bit PORT (
    A0 : IN STD_LOGIC;
    A1 : IN STD_LOGIC;
    A2 : IN STD_LOGIC;
    B0 : IN STD_LOGIC;
    B1 : IN STD_LOGIC;

```

```

    B2 : IN STD_LOGIC;

    C_in : IN STD_LOGIC;

    S0 : OUT STD_LOGIC;

    S1 : OUT STD_LOGIC;

    S2 : OUT STD_LOGIC;

    C_out : OUT STD_LOGIC);
END COMPONENT;

COMPONENT Register_Bank PORT (
    Reg_En : IN STD_LOGIC_VECTOR(2 DOWNTO 0);
    Clk : IN STD_LOGIC;
    A : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
    Reg_Bank_En : IN STD_LOGIC;
    Reset : IN STD_LOGIC;
    B0 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B1 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B2 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B3 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B4 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B5 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B6 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);
    B7 : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END COMPONENT;

COMPONENT ProgramRom PORT (
    Mem_address : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
    Instruction : OUT STD_LOGIC_VECTOR (11 DOWNTO 0));
END COMPONENT;

COMPONENT Mux_2_to_1_3bit PORT (
    S : IN STD_LOGIC;
    A : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
    B : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
    X : OUT STD_LOGIC_VECTOR (2 DOWNTO 0));
END COMPONENT;

COMPONENT Mux_2_to_1_4bit PORT (
    S : IN STD_LOGIC;
    A : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    B : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    X : OUT STD_LOGIC_VECTOR (3 DOWNTO 0));
END COMPONENT;

COMPONENT Mux_8_to_1_4bit PORT (
    S : IN STD_LOGIC_VECTOR(2 DOWNTO 0);

```

```

    A : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    B : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    C : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    D : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    E : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    F : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    G : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    H : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    X : OUT STD_LOGIC_VECTOR (3 DOWNTO 0));

END COMPONENT;

COMPONENT Slow_Clk PORT (
    Clk_in : IN STD_LOGIC;
    Clk_out : OUT STD_LOGIC);

END COMPONENT;

COMPONENT LUT_16_7 PORT (
    address : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
    data : OUT STD_LOGIC_VECTOR (6 DOWNTO 0));

END COMPONENT;

SIGNAL Imd_val_out : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Output of InstructionDecoder: Immediate value
SIGNAL Reg_en_out : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of InstructionDecoder: Register enable
SIGNAL Reg_selA_out : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of InstructionDecoder: Register select A
SIGNAL Load_sel_out : STD_LOGIC; -- Output of InstructionDecoder: Load select
SIGNAL Reg_selB_out : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of InstructionDecoder: Register select B
--SIGNAL MUX_EN_A_out : STD_LOGIC; -- Output of InstructionDecoder: Multiplexer A enable
--SIGNAL MUX_EN_B_out : STD_LOGIC; -- Output of InstructionDecoder: Multiplexer B enable
SIGNAL REG_BANK_EN_out : STD_LOGIC; -- Output of InstructionDecoder: Register bank enable
--SIGNAL Mux_2_to_1_EN_out : STD_LOGIC; -- Output of InstructionDecoder: Multiplexer 2-to-1 enable
SIGNAL Add_sub_sel_out : STD_LOGIC; -- Output of InstructionDecoder: Add/subtract select
SIGNAL Jump_address_out : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of InstructionDecoder: Jump address
SIGNAL Jump_out : STD_LOGIC; -- Output of InstructionDecoder: Jump

SIGNAL PC_out : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of PC: Current address
SIGNAL S4bit : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Outputs of Add_Sub: Sum bits
SIGNAL Zero_flag, Sign_flag, Overflow_flag, Carry_flag : STD_LOGIC; -- Outputs of Add_Sub: Flags
SIGNAL Counter : STD_LOGIC_VECTOR(2 DOWNTO 0); -- output of 3bit adder
SIGNAL C_out : STD_LOGIC; -- Output of adder_3bit: Carry-out

SIGNAL RB0, RB1, RB2, RB3, RB4, RB5, RB6, RB7 : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Outputs of Register_Bank: Register
values

SIGNAL Instruction : STD_LOGIC_VECTOR(11 DOWNTO 0); -- Output of ProgramRom: Instruction
SIGNAL X_2_Way_3bit : STD_LOGIC_VECTOR(2 DOWNTO 0); -- Output of Mux_2_to_1_3bit: Selected input
SIGNAL X_2_way_4bit : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Output of Mux_2_to_1_4bit: Selected input

```

```

SIGNAL X_8_way_4bitA : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Output of Mux_8_to_1_4bit A : Selected input
SIGNAL X_8_way_4bitB : STD_LOGIC_VECTOR(3 DOWNTO 0); -- Output of Mux_8_to_1_4bit B : Selected input
SIGNAL Clk_out : STD_LOGIC; -- Output of Slow_Clk: Slow clock
SIGNAL S_7Seg_out : STD_LOGIC_VECTOR(6 DOWNTO 0);

```

```

BEGIN

```

```

    LUT : LUT_16_7 PORT MAP(
        address => RB7,
        data => S_7Seg_out
    );

```

```

    InstructionDecoder_0 : InstructionDecoder PORT MAP(
        -- Port map connections
        Instruction => Instruction,
        Jump_sel => X_8_way_4bitA,
        Imd_val => Imd_val_out,
        Reg_en => Reg_en_out,
        Reg_selA => Reg_selA_out,
        Load_sel => Load_sel_out,
        Reg_selB => Reg_selB_out,
        --MUX_EN_A => MUX_EN_A_out,
        --MUX_EN_B => MUX_EN_B_out,
        REG_BANK_EN => REG_BANK_EN_out,
        --Mux_2_to_1_EN => Mux_2_to_1_EN_out,
        Add_sub_sel => Add_sub_sel_out,
        Jump_address => Jump_address_out,
        Jump => Jump_out
    );

```

```

    PC_0 : PC PORT MAP(
        -- Port map connections
        D_in => X_2_Way_3bit,
        Res => Res,
        Clk => Clk_out,
        Q_out => PC_out
    );

```

```

    Add_Sub_0 : Add_Sub PORT MAP(
        -- Port map connections
        M => Add_sub_sel_out,
        A0 => X_8_way_4bitA(0),
        A1 => X_8_way_4bitA(1),
        A2 => X_8_way_4bitA(2),
        A3 => X_8_way_4bitA(3),

```

```

    B0 => X_8_way_4bitB(0),
    B1 => X_8_way_4bitB(1),
    B2 => X_8_way_4bitB(2),
    B3 => X_8_way_4bitB(3),
    S0 => S4bit(0),
    S1 => S4bit(1),
    S2 => S4bit(2),
    S3 => S4bit(3),
    Zero_flag => Zero_flag,
    Sign_flag => Sign_flag,
    Overflow_flag => Overflow_flag,
    Carry_flag => Carry_flag
);

adder_3bit_0 : adder_3bit PORT MAP(
    A0 => PC_out(0),
    A1 => PC_out(1),
    A2 => PC_out(2),
    B0 => '0',
    B1 => '0',
    B2 => '0',
    C_in => '1',
    S0 => Counter(0),
    S1 => Counter(1),
    S2 => Counter(2),
    C_out => C_out
);

Register_Bank_0 : Register_Bank PORT MAP(
    -- Port map connections
    Reg_En => Reg_en_out,
    Clk => Clk_out,
    A => X_2_way_4bit,
    Reg_Bank_En => REG_BANK_EN_out,
    Reset => Res,
    B0 => RB0,
    B1 => RB1,
    B2 => RB2,
    B3 => RB3,
    B4 => RB4,
    B5 => RB5,
    B6 => RB6,
    B7 => RB7
);

```

```

ProgramRom_0 : ProgramRom PORT MAP(
    -- Port map connections
    Mem_Address => PC_out,
    Instruction => Instruction
);

Mux_2_to_1_3bit_0 : Mux_2_to_1_3bit PORT MAP(
    -- Port map connections
    S => Jump_out,
    A => Jump_address_out,
    B => Counter,
    X => X_2_Way_3bit
);

Mux_2_to_1_4bit_0 : Mux_2_to_1_4bit PORT MAP(
    -- Port map connections
    S => Load_sel_out,
    A => Imd_val_out,
    B => S4bit,
    X => X_2_way_4bit
);

Mux_8_to_1_4bit_A : Mux_8_to_1_4bit PORT MAP(
    -- Port map connections
    S => Reg_selA_out,
    A => RB0,
    B => RB1,
    C => RB2,
    D => RB3,
    E => RB4,
    F => RB5,
    G => RB6,
    H => RB7,
    X => X_8_way_4bitA
);

Mux_8_to_1_4bit_B : Mux_8_to_1_4bit PORT MAP(
    -- Port map connections
    S => Reg_selB_out,
    A => RB0,
    B => RB1,
    C => RB2,
    D => RB3,
    E => RB4,
    F => RB5,

```



```

        G => RB6,
        H => RB7,
        X => X_8_way_4bitB
    );

    Slow_Clk_0 : Slow_Clk PORT MAP(
        Clk_in => Clk,
        Clk_out => Clk_out
    );

    OUT_REG <= RB7;
    Overflow <= Overflow_flag;
    Zero <= Zero_flag;
    S_7Seg <= S_7Seg_out;
    Anode <= "1110";

END Behavioral;

```

## LUT\_16\_7

```

-----
--
-- Company:
-- Engineer:
--
-- Create Date: 06/08/2023 01:36:19 AM
-- Design Name:
-- Module Name: LUT_16 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

use ieee.numeric_std.all;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity LUT_16_7 is
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end LUT_16_7;

architecture Behavioral of LUT_16_7 is
    type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);

    signal sevenSegment_ROM : rom_type := (
        "1000000", -- 0
        "1111001", -- 1
        "0100100", -- 2
        "0110000", -- 3
        "0110001", -- 4
        "0010010", -- 5
        "0000010", -- 6
        "1111000", -- 7
        "0000000", -- 8
        "0010000", -- 9
        "0001000", -- a
        "0000011", -- b
        "1000110", -- c
        "0100001", -- d
        "0000110", -- e
        "0001110" -- f
    );
begin
    data <= sevenSegment_ROM(to_integer(unsigned(address)));
end Behavioral;

```

## Instruction Decoder

```
-----  
-  
-- Company:  
-- Engineer:  
--  
-- Create Date: 06/05/2023 11:22:34 PM  
-- Design Name:  
-- Module Name: Instruction_Decoder - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
-  
  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
ENTITY InstructionDecoder IS  
    PORT (  
        Instruction : IN STD_LOGIC_VECTOR (11 DOWNTO 0);  
        Jump_sel : IN STD_LOGIC_VECTOR(3 DOWNTO 0);  
        Imd_val : OUT STD_LOGIC_VECTOR(3 DOWNTO 0);  
        Reg_en : OUT STD_LOGIC_VECTOR(2 DOWNTO 0);  
        Reg_selA : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);  
        Load_sel : OUT STD_LOGIC;  
        Reg_selB : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);  
        --MUX_EN_A : OUT STD_LOGIC;  
        --MUX_EN_B : OUT STD_LOGIC;  
        REG_BANK_EN : OUT STD_LOGIC;  
        --Mux_2_to_1_EN : OUT STD_LOGIC;  
        Add_sub_sel : OUT STD_LOGIC;  
        Jump_address : OUT STD_LOGIC_VECTOR (2 DOWNTO 0);  
        Jump : OUT STD_LOGIC);  
END;
```

```

END InstructionDecoder;

ARCHITECTURE Behavioral OF InstructionDecoder IS

BEGIN

    PROCESS (Instruction, Jump_Sel)
    BEGIN

        -- MUX_EN_A <= '0';
        --MUX_EN_B <= '0';
        REG_BANK_EN <= '0';
        Jump <= '0';

        IF (Instruction(11 DOWNT0 10) = "00") THEN -- add
            -- MUX_EN_A <= '1';
            -- MUX_EN_B <= '1';
            Reg_selA <= Instruction(9 DOWNT0 7);
            Reg_selB <= Instruction(6 DOWNT0 4);
            Add_sub_sel <= '0';
            -- Mux_2_to_1_EN <= '1';
            Load_sel <= '0';
            REG_BANK_EN <= '1';
            Reg_en <= Instruction(9 DOWNT0 7);

        ELSIF (Instruction(11 DOWNT0 10) = "01") THEN -- neg
            -- MUX_EN_A <= '1';
            --MUX_EN_B <= '1';
            Reg_selA <= "000";
            Reg_selB <= Instruction(9 DOWNT0 7);
            Add_sub_sel <= '1';
            --Mux_2_to_1_EN <= '1';
            Load_sel <= '0';
            REG_BANK_EN <= '1';
            Reg_en <= Instruction(9 DOWNT0 7);

        ELSIF (Instruction(11 DOWNT0 10) = "10") THEN --movi
            REG_BANK_EN <= '1';
            Reg_en <= Instruction(9 DOWNT0 7);
            --Mux_2_to_1_EN <= '1';
            Load_sel <= '1';
            Imd_val <= Instruction(3 DOWNT0 0);

        ELSIF (Instruction(11 DOWNT0 10) = "11") THEN --jump
            -- JZR R1, 7 ; If R1 = 0 jump to line 7 format: 11 RRR 0000 ddd

```

```

        Reg_selA <= Instruction(9 DOWNT0 7); -- GET THE VALUE OF THE REGISTER
RRR IN THE REGISTER A
        IF (Jump_sel = "0000") THEN
            Jump <= '1'; -- set jump flag
            Jump_address <= Instruction(2 DOWNT0 0);
        END IF;

    END IF;
END PROCESS;
END Behavioral;

```

## Program Counter

```

-----
-
-- Company:
-- Engineer:
--
-- Create Date: 05/23/2023 03:58:14 PM
-- Design Name:
-- Module Name: PC - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;

```

```

--use UNISIM.VComponents.all;

ENTITY PC IS
    PORT (
        D_in : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
        Res : IN STD_LOGIC;
        Clk : IN STD_LOGIC;
        Q_out : OUT STD_LOGIC_VECTOR (2 DOWNTO 0));
END PC;

ARCHITECTURE Behavioral OF PC IS
    COMPONENT D_FF
        PORT (
            D : IN STD_LOGIC;
            Res : IN STD_LOGIC;
            Clk : IN STD_LOGIC;
            Q : OUT STD_LOGIC);
    END COMPONENT;

BEGIN

    D_FF0 : D_FF
    PORT MAP(
        D => D_in(0),
        Res => Res,
        Clk => Clk,
        Q => Q_out(0)
    );

    D_FF1 : D_FF
    PORT MAP(
        D => D_in(1),
        Res => Res,
        Clk => Clk,
        Q => Q_out(1)
    );

    D_FF2 : D_FF
    PORT MAP(
        D => D_in(2),
        Res => Res,
        Clk => Clk,
        Q => Q_out(2)
    );
END Behavioral;

```

## Adder\ Substracter

```
-----  
--  
-- Company:  
-- Engineer:  
--  
-- Create Date: 03/16/2023 11:47:57 AM  
-- Design Name:  
-- Module Name: RCA_4 - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
--  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
ENTITY Add_Sub IS  
    PORT (  
        M : IN STD_LOGIC;  
        A0 : IN STD_LOGIC;  
        A1 : IN STD_LOGIC;  
        A2 : IN STD_LOGIC;
```

```

        A3 : IN STD_LOGIC;
        B0 : IN STD_LOGIC;
        B1 : IN STD_LOGIC;
        B2 : IN STD_LOGIC;
        B3 : IN STD_LOGIC;
        S0 : OUT STD_LOGIC;
        S1 : OUT STD_LOGIC;
        S2 : OUT STD_LOGIC;
        S3 : OUT STD_LOGIC;
        Zero_flag : OUT STD_LOGIC;
        Sign_flag : OUT STD_LOGIC;
        Overflow_flag : OUT STD_LOGIC;
        Carry_flag : OUT STD_LOGIC
    );
END Add_Sub;

ARCHITECTURE Behavioral OF Add_Sub IS
    COMPONENT FA
        PORT (
            A : IN STD_LOGIC;
            B : IN STD_LOGIC;
            C_in : IN STD_LOGIC;
            S : OUT STD_LOGIC;
            C_out : OUT STD_LOGIC);
    END COMPONENT;

    SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C, FA3_S, FA3_C : STD_LOGIC;
    SIGNAL NB0, NB1, NB2, NB3 : STD_LOGIC;
    SIGNAL S : STD_LOGIC_VECTOR(3 DOWNTO 0);

BEGIN

    NB0 <= (B0 XOR M);
    NB1 <= (B1 XOR M);
    NB2 <= (B2 XOR M);
    NB3 <= (B3 XOR M);

    FA_0 : FA
    PORT MAP(
        A => A0,
        B => NB0,
        C_in => M,
        S => S(0),
        C_Out => FA0_C);

```



```

FA_1 : FA
PORT MAP(
    A => A1,
    B => NB1,
    C_in => FA0_C,
    S => S(1),
    C_Out => FA1_C);

FA_2 : FA
PORT MAP(
    A => A2,
    B => NB2,
    C_in => FA1_C,
    S => S(2),
    C_Out => FA2_C);
FA_3 : FA
PORT MAP(
    A => A3,
    B => NB3,
    C_in => FA2_C,
    S => S(3),
    C_Out => Carry_flag);
S0 <= S(0);
S1 <= S(1);
S2 <= S(2);
S3 <= S(3);

Zero_flag <= (NOT S(0)) AND (NOT S(1)) AND (NOT S(2)) AND (NOT S(3));

Sign_flag <= S(3);

Overflow_flag <= (NOT M) AND (A3 XNOR B3) AND (A3 XOR S(3));

END Behavioral;

```

## Adder\_3bit

```

-----
--
-- Company:
-- Engineer:
--
-- Create Date: 05/23/2023 03:41:39 PM
-- Design Name:

```

```

-- Module Name: RCA_3 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

ENTITY Adder_3bit IS
    PORT (
        A0 : IN STD_LOGIC;
        A1 : IN STD_LOGIC;
        A2 : IN STD_LOGIC;

        B0 : IN STD_LOGIC;
        B1 : IN STD_LOGIC;
        B2 : IN STD_LOGIC;

        C_in : IN STD_LOGIC;
        S0 : OUT STD_LOGIC;
        S1 : OUT STD_LOGIC;
        S2 : OUT STD_LOGIC;

        C_out : OUT STD_LOGIC);
END Adder_3bit;

ARCHITECTURE Behavioral OF Adder_3bit IS

```

```

COMPONENT FA
  PORT (
    A : IN STD_LOGIC;
    B : IN STD_LOGIC;
    C_in : IN STD_LOGIC;
    S : OUT STD_LOGIC;
    C_out : OUT STD_LOGIC);
END COMPONENT;

SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C : STD_LOGIC;

BEGIN
  FA_0 : FA
  PORT MAP(
    A => A0,
    B => B0,
    C_in => C_in,
    S => S0,
    C_Out => FA0_C);

  FA_1 : FA
  PORT MAP(
    A => A1,
    B => B1,
    C_in => FA0_C,
    S => S1,
    C_Out => FA1_C);

  FA_2 : FA
  PORT MAP(
    A => A2,
    B => B2,
    C_in => FA1_C,
    S => S2,
    C_Out => C_out);
END Behavioral;

```

## Register Bank

```

-----
-
-- Company:
-- Engineer:
--

```

```

-- Create Date: 06/01/2023 04:31:10 PM
-- Design Name:
-- Module Name: Register_Bank - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Register_Bank is
    port (
        Reg_En: in std_logic_vector(2 downto 0);
        Clk: in std_logic;
        A: in std_logic_vector(3 downto 0);
        Reg_Bank_En: in std_logic;
        Reset: in std_logic;
        B0: out std_logic_vector(3 downto 0);
        B1: out std_logic_vector(3 downto 0);
        B2: out std_logic_vector(3 downto 0);
        B3: out std_logic_vector(3 downto 0);
        B4: out std_logic_vector(3 downto 0);
        B5: out std_logic_vector(3 downto 0);
        B6: out std_logic_vector(3 downto 0);
        B7: out std_logic_vector(3 downto 0)
    );
end entity Register_Bank;

```

```

    );
end Register_Bank;

architecture Behavioral of Register_Bank is
component Reg
    port(
        D : in STD_LOGIC_VECTOR (3 downto 0);
        En : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Res : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0)
    );
end component;

component Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
           EN : in STD_LOGIC;
           Y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

    signal YB : std_logic_vector(7 downto 0);

begin
    Decoder_3_to_8_1 : Decoder_3_to_8 port map(
        I => Reg_En,
        EN => Reg_Bank_En,
        Y => YB
    );

    R0: Reg port map(
        D => "0000",
        En => '1',
        Clk => Clk,
        Res => Reset,
        Q => B0
    );

    R1: Reg port map(
        D => A,
        En => YB(1),
        Clk => Clk,
        Res => Reset,
        Q => B1
    );

    R2: Reg port map(

```

```
    D => A,  
    En => YB(2),  
    Clk => Clk,  
    Res => Reset,  
    Q => B2  
);  
R3: Reg port map(  
    D => A,  
    En => YB(3),  
    Clk => Clk,  
    Res => Reset,  
    Q => B3  
);  
R4: Reg port map(  
    D => A,  
    En => YB(4),  
    Clk => Clk,  
    Res => Reset,  
    Q => B4  
);  
R5: Reg port map(  
    D => A,  
    En => YB(5),  
    Clk => Clk,  
    Res => Reset,  
    Q => B5  
);  
R6: Reg port map(  
    D => A,  
    En => YB(6),  
    Clk => Clk,  
    Res => Reset,  
    Q => B6  
);  
R7: Reg port map(  
    D => A,  
    En => YB(7),  
    Clk => Clk,  
    Res => Reset,  
    Q => B7  
);  
  
end Behavioral;
```

## Program ROM

```
-----  
-  
-- Company:  
-- Engineer:  
--  
-- Create Date: 06/06/2023 01:52:25 PM  
-- Design Name:  
-- Module Name: Program_ROM - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
-  
  
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
USE IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
ENTITY ProgramRom IS  
    PORT (  
        Mem_address : IN STD_LOGIC_VECTOR (2 DOWNTO 0);  
        Instruction : OUT STD_LOGIC_VECTOR (11 DOWNTO 0));  
END ProgramRom;  
  
ARCHITECTURE Behavioral OF ProgramRom IS  
    TYPE rom_type IS ARRAY (0 TO 7) OF STD_LOGIC_VECTOR(11 DOWNTO 0);  
    SIGNAL progam_ROM : rom_type := (  
        "100100000011", --MOVI R2, 3  
        10 RRR 000 0011
```

```

    "101110000000", --MOVI R7, 0          10 RRR 000 0000
    "101000001111", --MOVI R4, -1         10 RRR 000 1110
    "001110100000", --ADD R7, R2          00 RRR RRR 0000
    "000101000000", --ADD R2, R4          00 RRR RRR 0000
    "110100000111", --JZR R2, 8           11 RRR 0000 111
    "110000000011", --JZR R0,4           11 RRR 0000 100
    "001110000000" --ADD R7, R0          00 RRR RRR 0000
);

BEGIN
    Instruction <= program_ROM(to_integer(unsigned(Mem_address)));
END Behavioral;

```

## 2 way 3 bit MUX

```

-----
-
-- Company:
-- Engineer:
--
-- Create Date: 05/31/2023 12:11:03 AM
-- Design Name:
-- Module Name: 2_way_3_bit_mux - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating

```



```

-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

ENTITY Mux_2_to_1_3bit IS
    PORT (
        S : IN STD_LOGIC;
        A : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
        X : OUT STD_LOGIC_VECTOR (2 DOWNTO 0));
END Mux_2_to_1_3bit;

ARCHITECTURE Behavioral OF Mux_2_to_1_3bit IS

BEGIN
    X <= A WHEN (S = '1') ELSE
    B;

END Behavioral;

```

## 2 way 4 bit MUX

```

-----
-
-- Company:
-- Engineer:
--
-- Create Date: 05/31/2023 12:36:47 AM
-- Design Name:
-- Module Name: Mux_2_to_1_4bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-
LIBRARY IEEE;

```

```

USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

ENTITY Mux_2_to_1_4bit IS
    PORT (
        S : IN STD_LOGIC;
        A : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        X : OUT STD_LOGIC_VECTOR (3 DOWNTO 0));
END Mux_2_to_1_4bit;

ARCHITECTURE Behavioral OF Mux_2_to_1_4bit IS

BEGIN
    X <= A WHEN (S = '1') ELSE
        B;

END Behavioral;

```

## 8 way 4 bit MUX

```

-----
-
-- Company:
-- Engineer:
--
-- Create Date: 05/31/2023 12:50:47 AM
-- Design Name:
-- Module Name: Mux_8_to_1_4bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool Versions:
-- Description:
--
-- Dependencies:
--

```

```

-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
-
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

ENTITY Mux_8_to_1_4bit IS
    PORT (
        S : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
        A : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        B : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        C : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        D : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        E : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        F : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        G : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        H : IN STD_LOGIC_VECTOR (3 DOWNTO 0);
        X : OUT STD_LOGIC_VECTOR (3 DOWNTO 0));
END Mux_8_to_1_4bit;

ARCHITECTURE Behavioral OF Mux_8_to_1_4bit IS

BEGIN
    WITH s SELECT
        X <= A WHEN "000",
        B WHEN "001",
        C WHEN "010",
        D WHEN "011",
        E WHEN "100",
        F WHEN "101",
        G WHEN "110",
        H WHEN OTHERS;

```

```
END behavioral;
```

## Slow Clock

```
-----  
--  
-- Company:  
-- Engineer:  
--  
-- Create Date: 04/04/2023 12:13:55 PM  
-- Design Name:  
-- Module Name: Slow_Clk - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool Versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
--  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx leaf cells in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity Slow_Clk is  
    Port ( Clk_in : in STD_LOGIC;  
          Clk_out : out STD_LOGIC);  
end Slow_Clk;
```

```

architecture Behavioral of Slow_Clk is


signal count : integer := 1;
signal Clk_status : std_logic := '0';

begin
    process(Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if (count = 1) then
                Clk_status <= not Clk_status;
                Clk_out <= Clk_status;
                count <= 1;
            end if;
        end if;
    end process;


end Behavioral;

```


## 2 WAY 3 BIT MUX

 


## 2 WAY 4 BIT MUX

 


## 8 WAY 4 BIT MUX

 


## Add\_Sub sim

 


## InstructionDecoder\_SIM

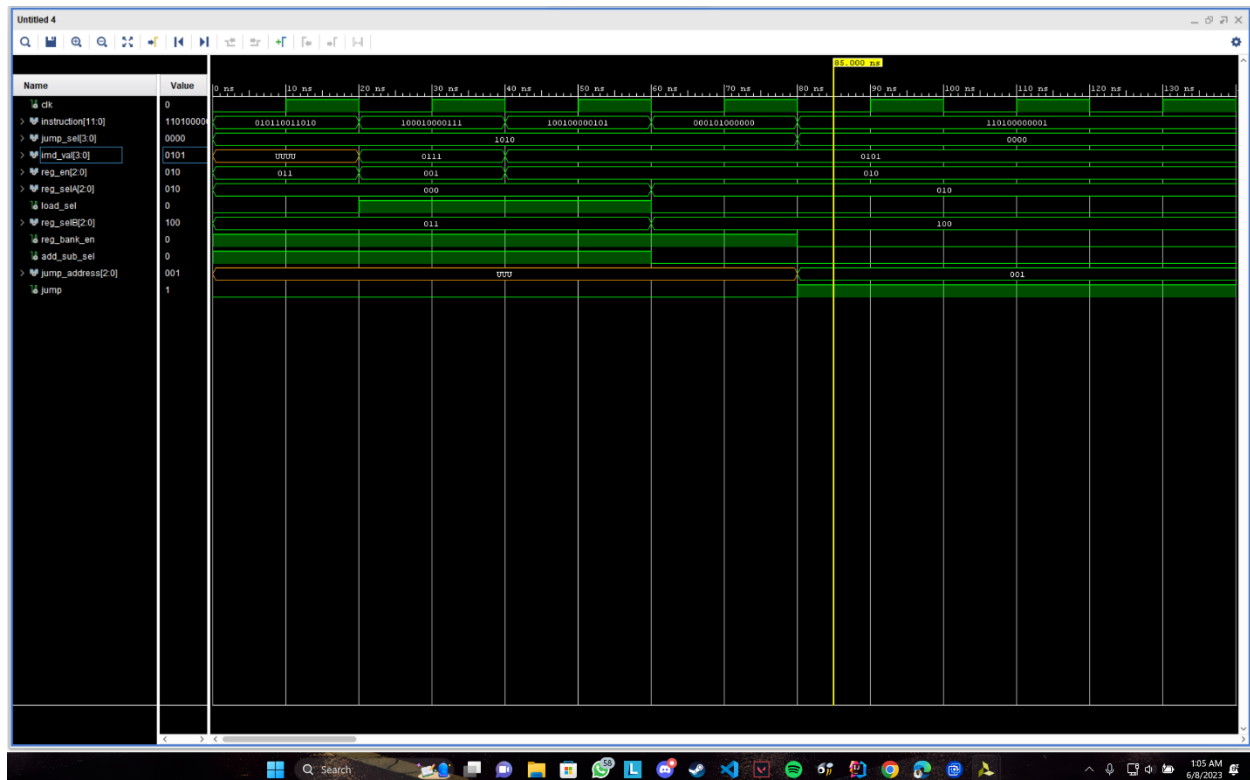

## Nano\_sim

 


## PC\_Sim

 



## Register\_Bank\_Sim

 

## Conclusion

In this lab, we designed and developed a 4-bit nanoprocessor that can execute four instructions: MOVI, ADD, NEG, and JZR. We used various components such as a 4-bit add/subtract unit, a 3-bit program counter, an 8-way 4-bit multiplexer, a register bank, a program ROM, and an instruction decoder. We tested our design using simulation and on the BASYS 3 board. We also wrote an assembly program to calculate the sum of integers from 1 to 3 and verified the result on R7. We learned how to apply the principles of computer organization and digital design to build a simple microprocessor and how to use VHDL to implement and test our circuits. Our experiment succeeded in meeting the learning outcomes of the lab.

## Team members

We shared the components and created them.

Gamage – Instruction Decoder, Program ROM, Register Bank, PC

Ninduwara – All MUXes, 2 Adders

After creating each component we discussed and made the nanoprocessor together.